

### MIPS processor continued


#### Review


- Different parts in the processor should be connected appropriately to be able to carry out the functions.
- Connections depending on what we need
- Learnt R-type, lw, sw, beq

### lw & sw?

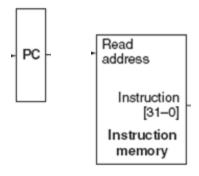


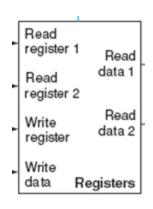

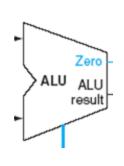

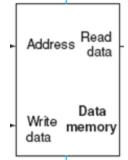


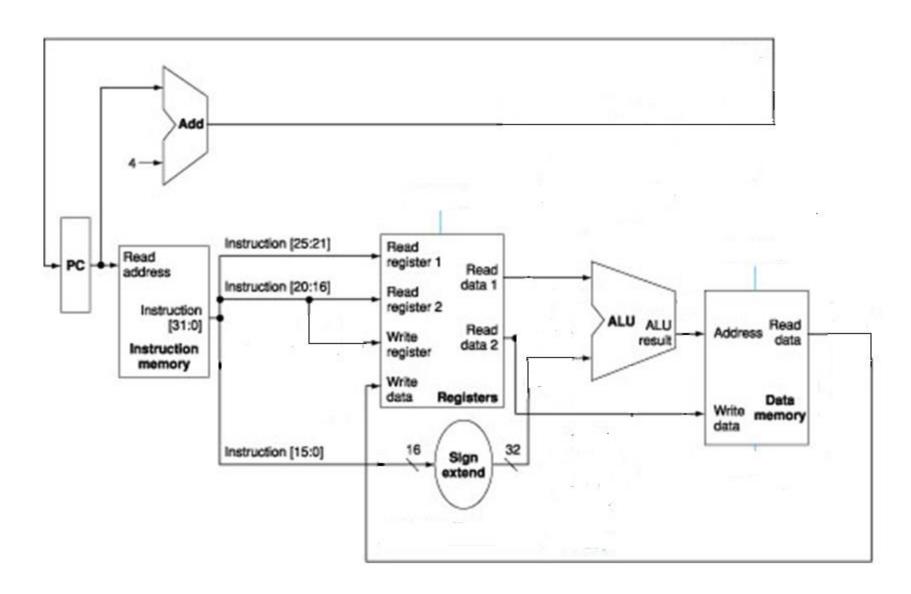
### Data path only for lw and sw (answer)




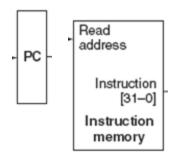
# Data path for both R-type and memory-type instructions

add \$rd, \$rs, \$rt, format: opcode (6 bits) rs (5 bits) rt (5 bits) rd (5 bits) 00000 funct (6 bits) lw \$rt, offset\_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits) sw \$rt, offset\_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits)



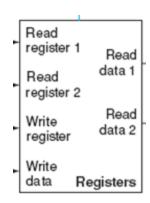


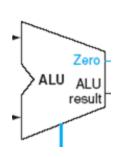

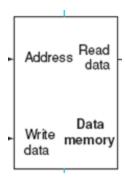

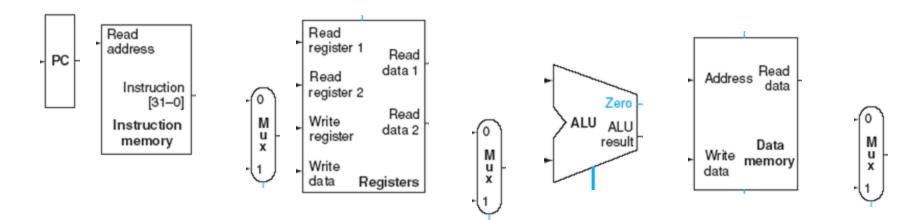
# Data path for both R-type and memory-type instructions


add \$rd, \$rs, \$rt, format: opcode (6 bits) rs (5 bits) rt (5 bits) rd (5 bits) 00000 funct (6 bits) lw \$rt, offset\_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits) sw \$rt, offset\_value(\$rs): opcode (6 bits) rs (5 bits) rt (5 bits) offset (16 bits)




#### **Answer**

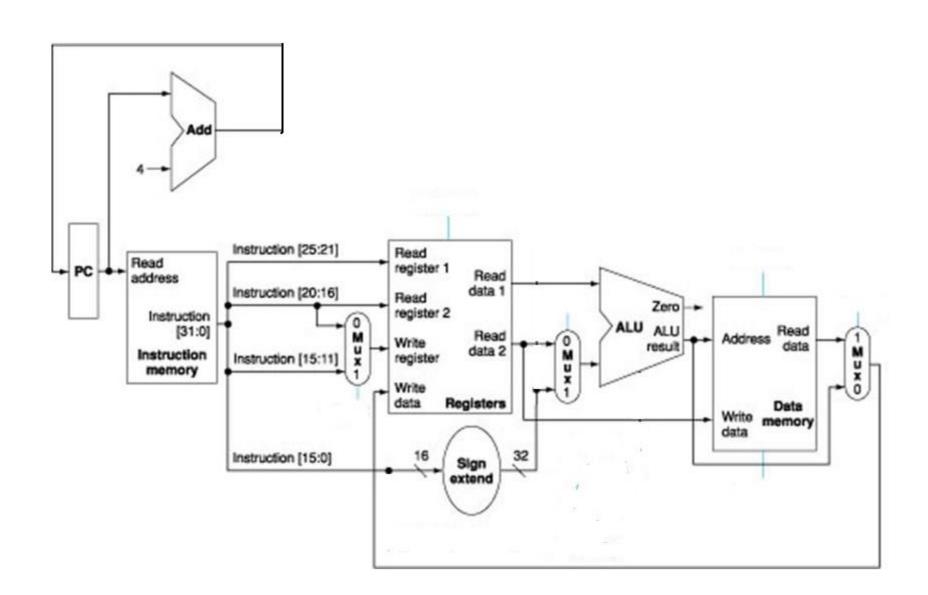

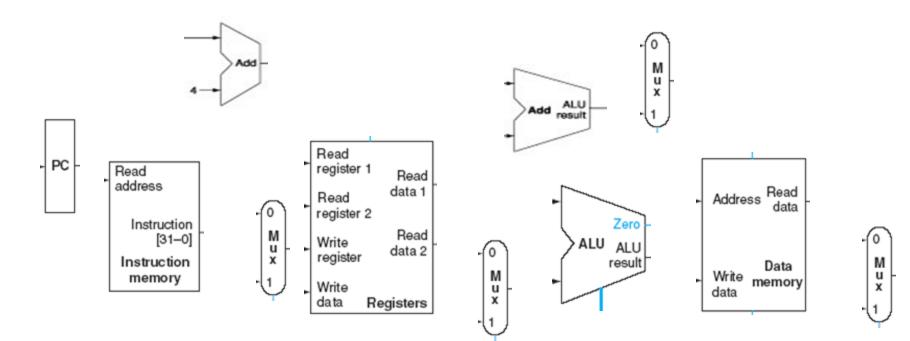
# Datapath for R-type, memory, and branch operations


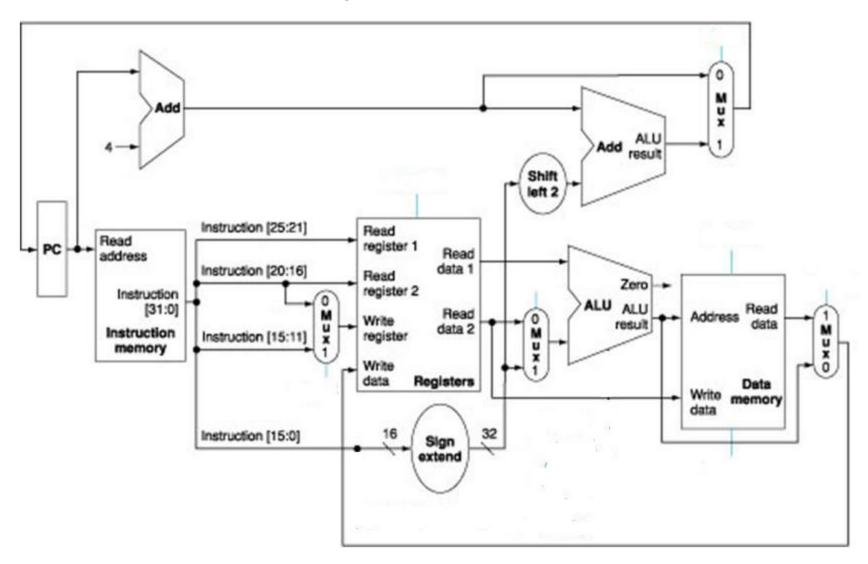
# Datapath for R-type, memory, and branch operations (Answer)


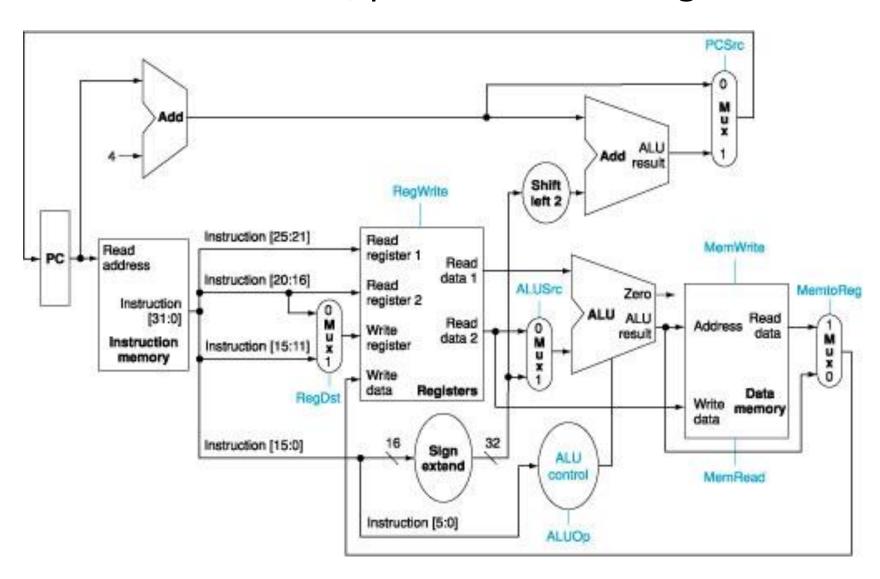
### Datapath for Memory, R-type and Branch Instructions, plus the control signals



### Jump Instruction

- Jump instruction seems easy to implement
  - We just need to replace the lower 28 bits of the
    PC with the lower 26 bits of the instruction shifted
    by 2 bits
    - The shift is achieved by simply concatenating 00 to the jump offset


### Implementing Jumps

- The one we have supports arithmetic/logic instructions, branch instructions, load and store instructions
  - We need also to support the jump instruction




— What are the changes we need to make?

#### Add j?

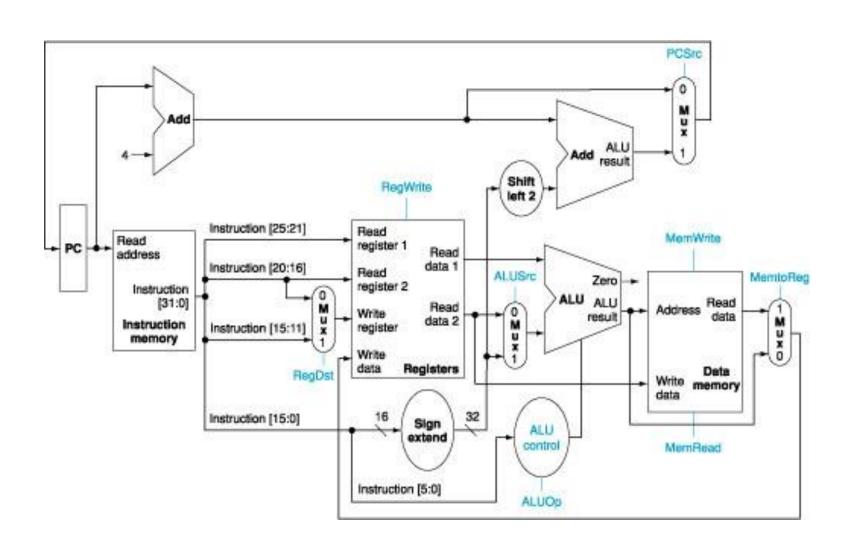


### Supporting Jump Instruction

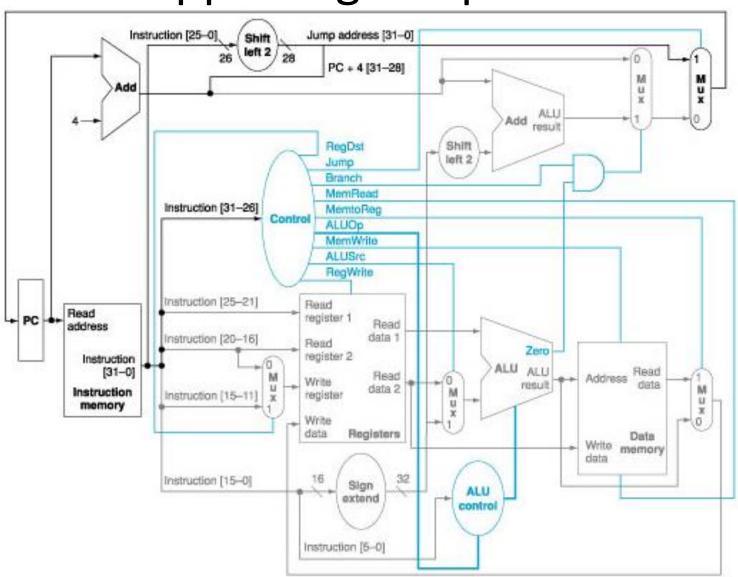

### In Class Exercise – Supporting Jump Register

#### Jump register

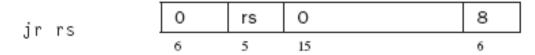

Unconditionally jump to the instruction whose address is in register rs.